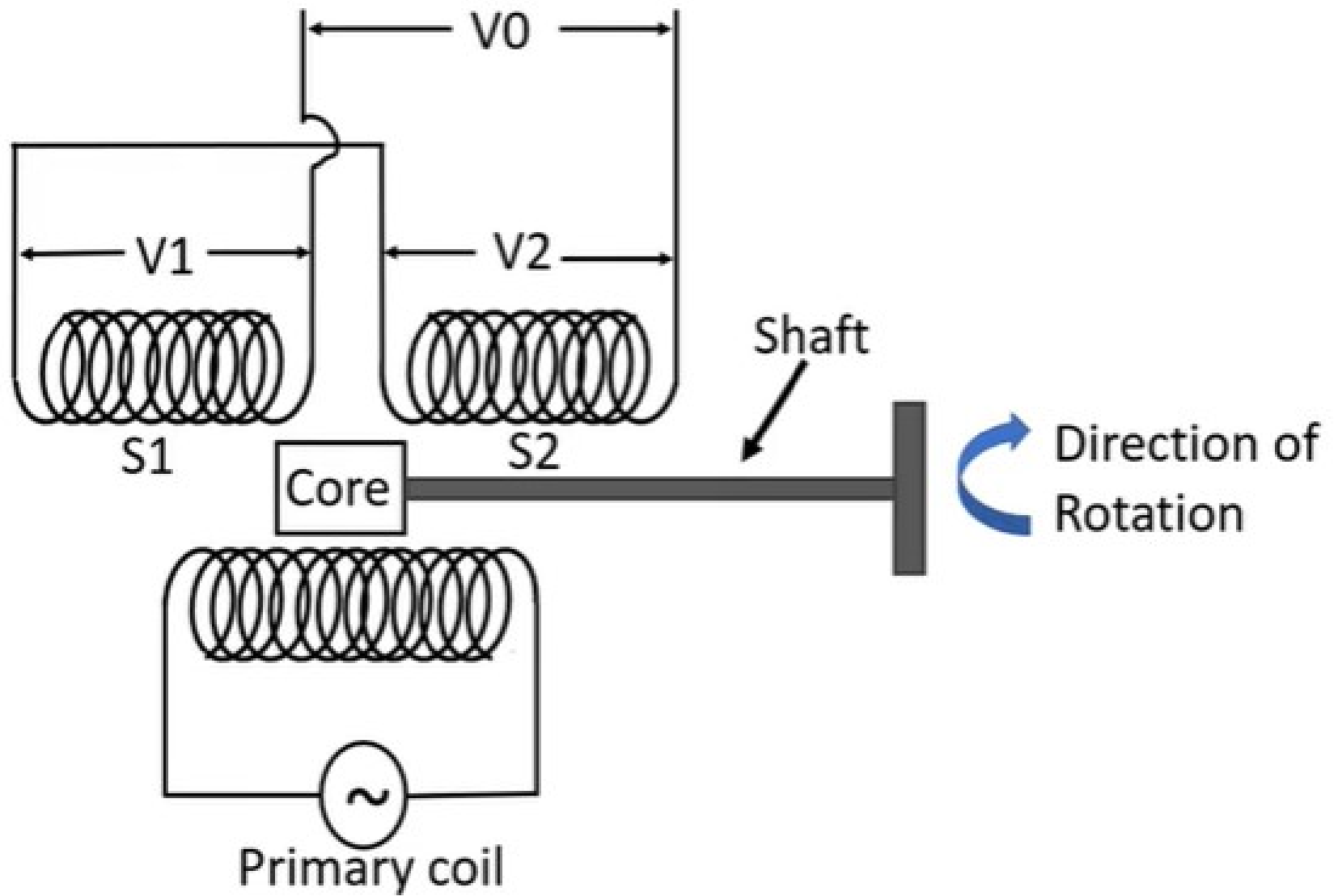


Rotary Variable Differential Transformer(RVDT)


Riya Jacob K

Assistant Professor on Contract
Dept of Computer Applications

Construction




Working of RVDT

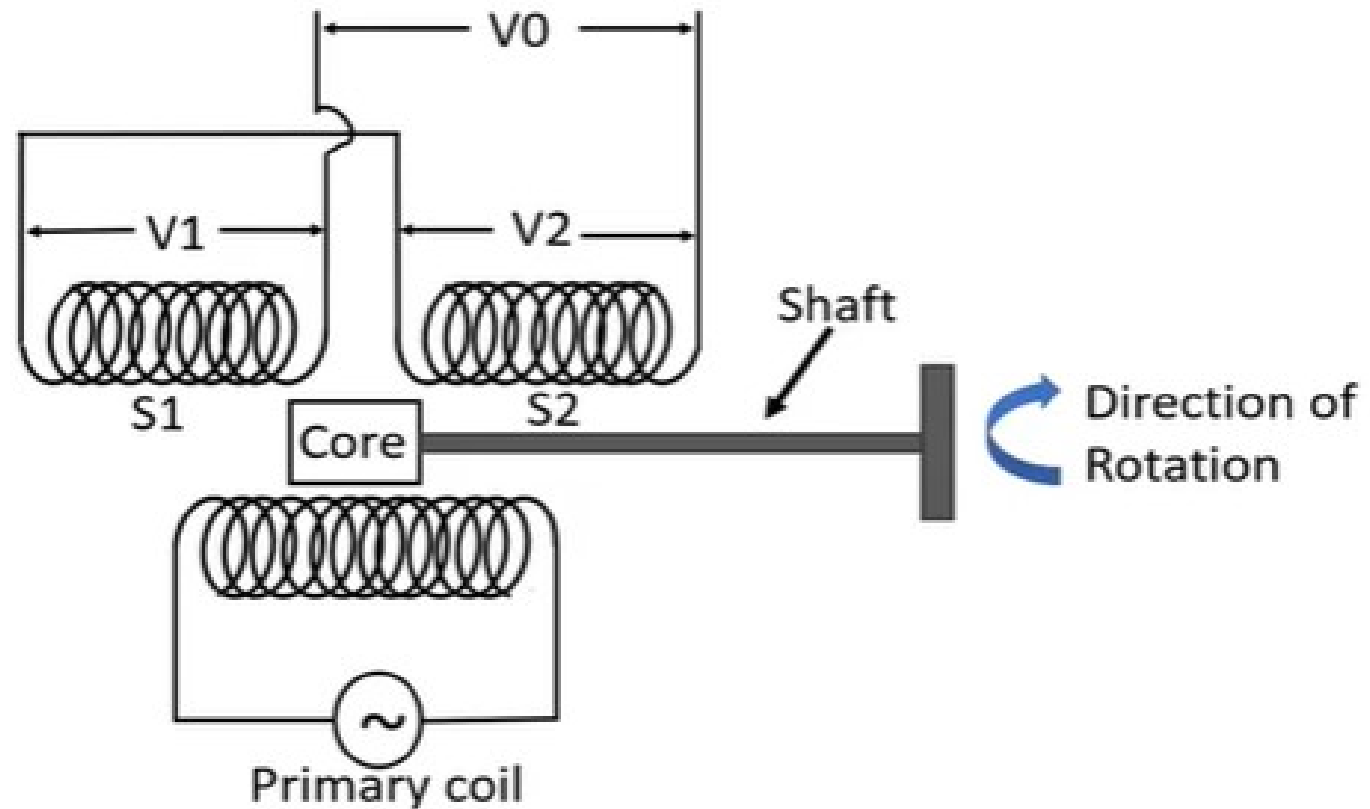

The differential output is $V_0 = V_1 - V_2$

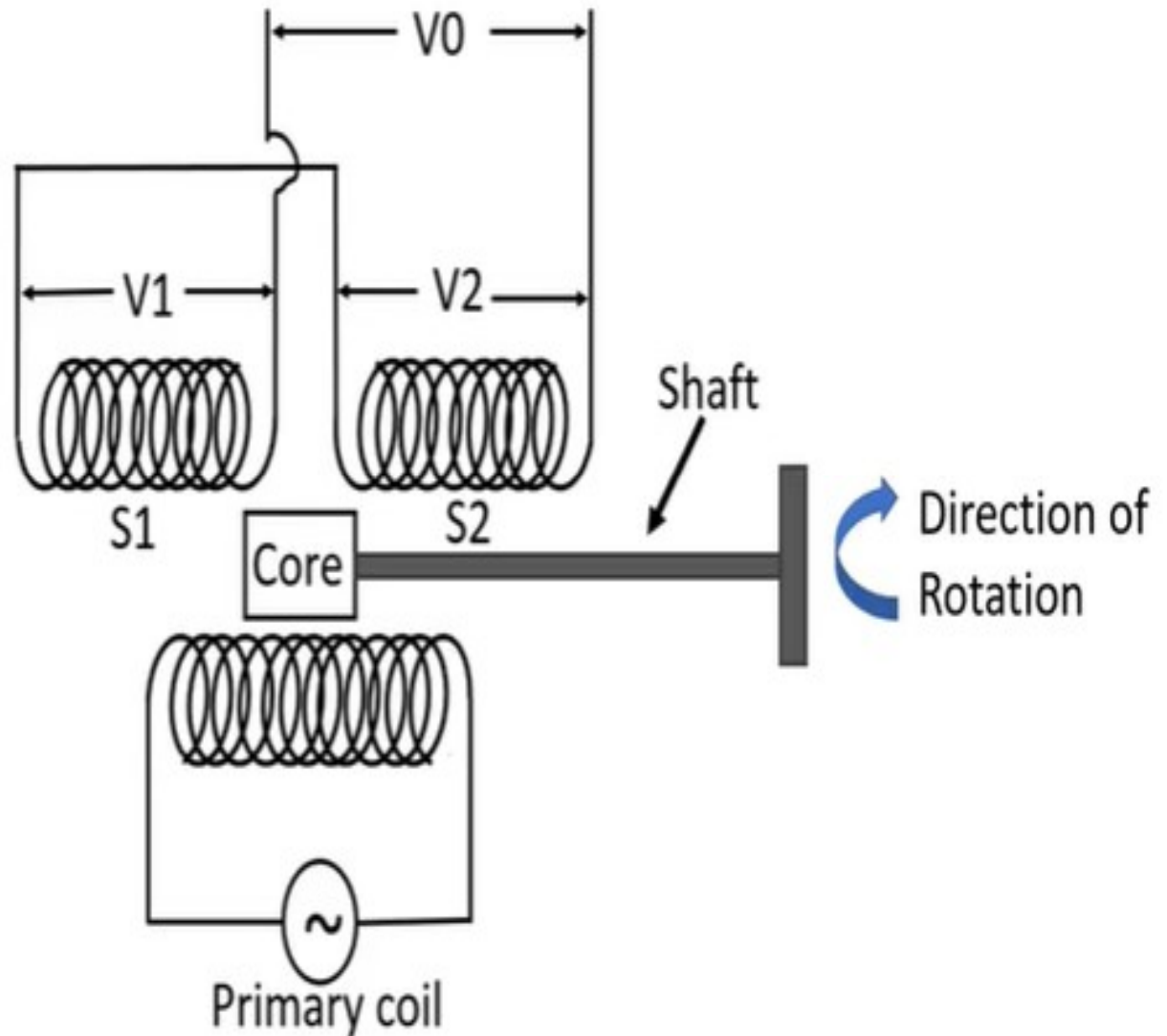
- CASE 1: The core is at centre of the secondary windings (for no displacement)




That is $V_1 = V_2$

$$V_0 = V_1 - V_2 = 0$$

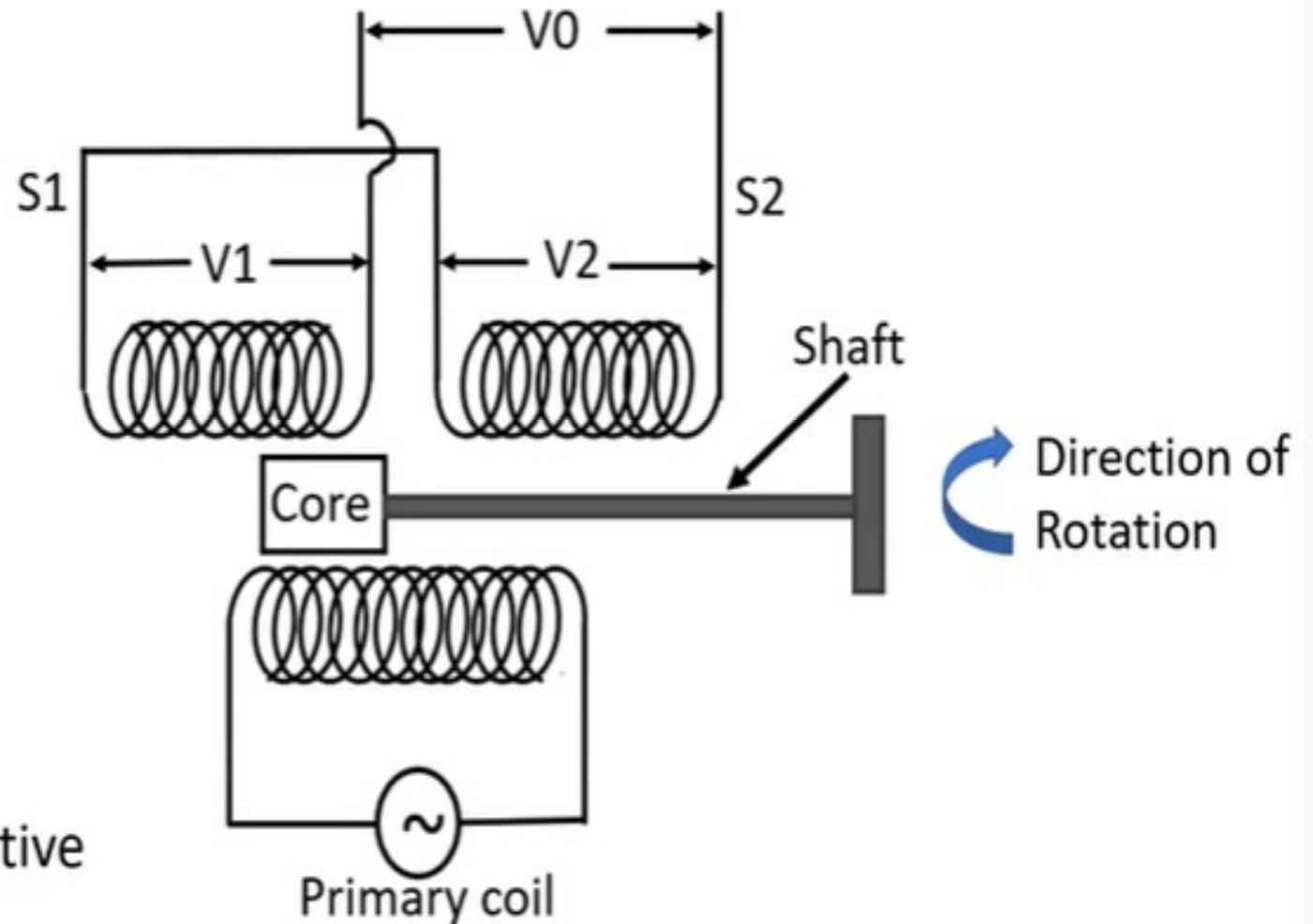- CASE 2: The core position is towards the S1 windings of the secondary (for clockwise movement)





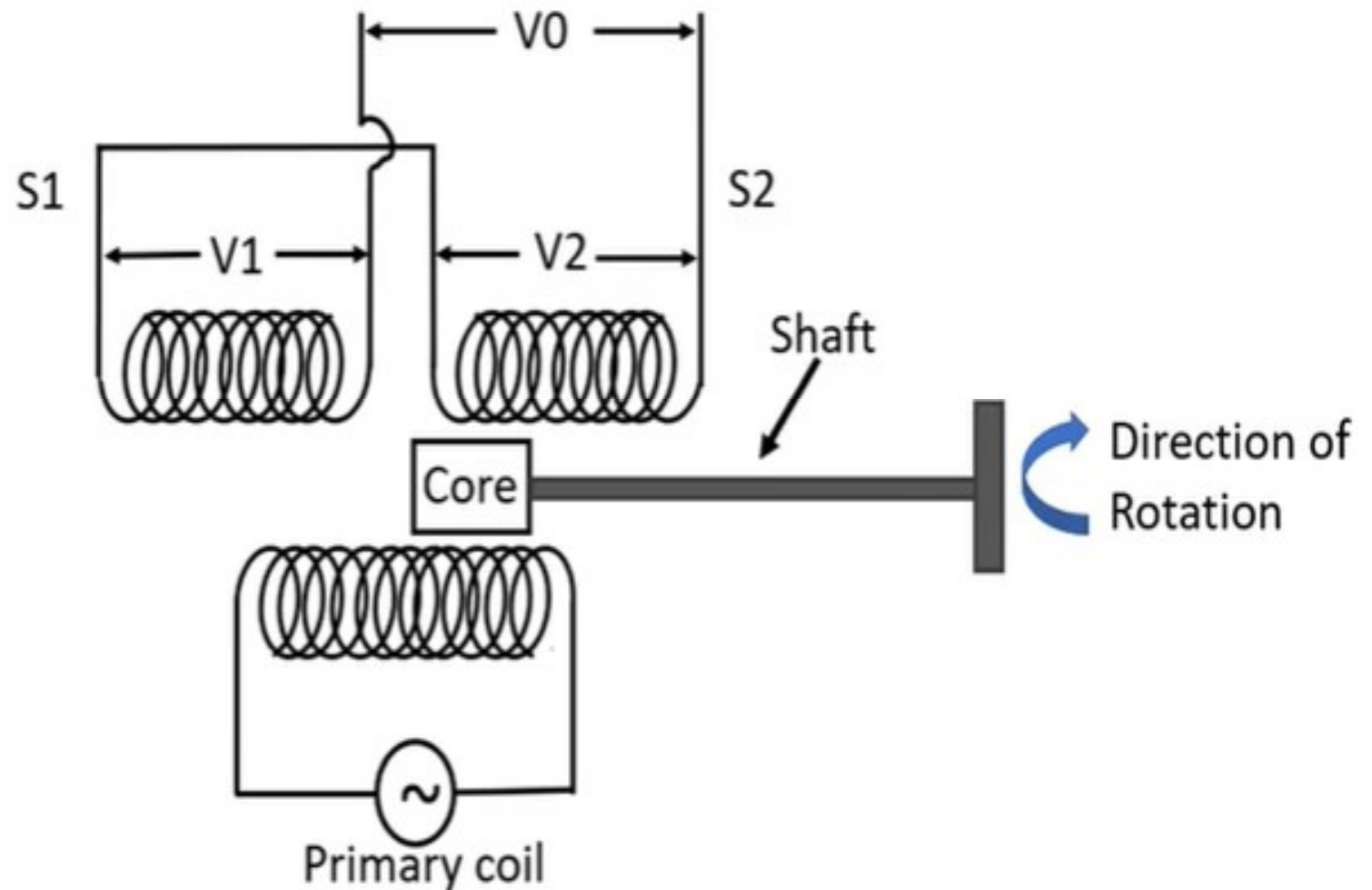- CASE 3: The core position is towards the S2 windings of the secondary (for anti-clockwise movement)



$V_2 > V_1$
 $V_0 = V_1 - V_2$
 is negative.

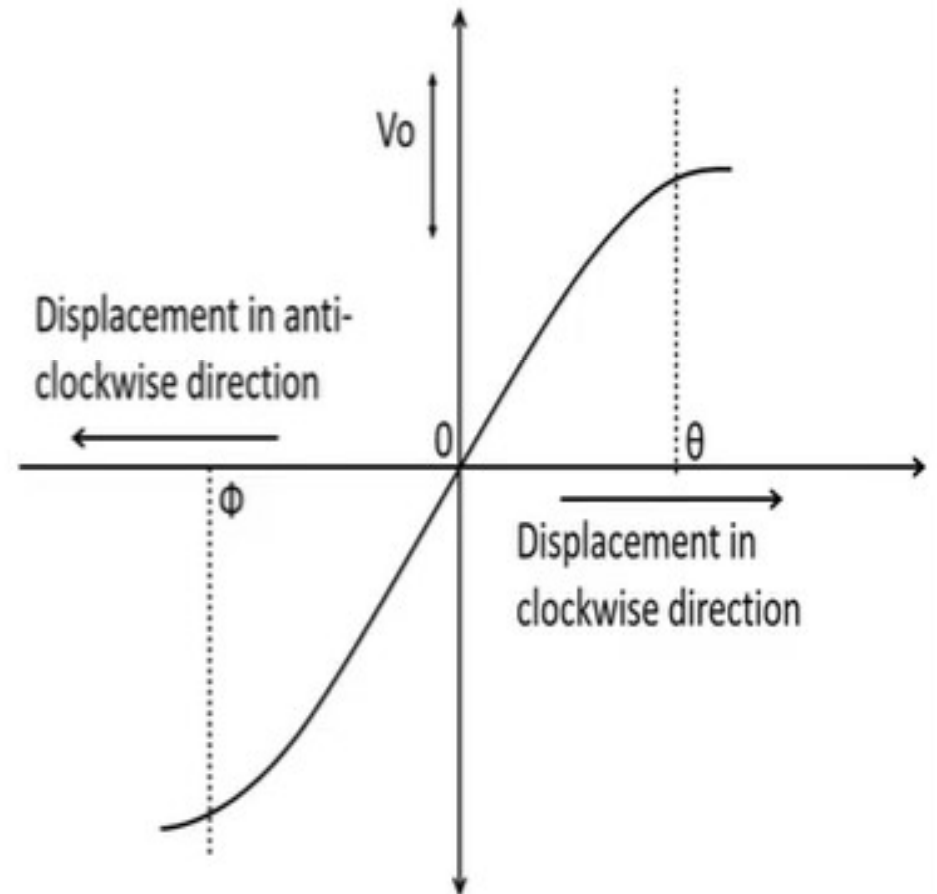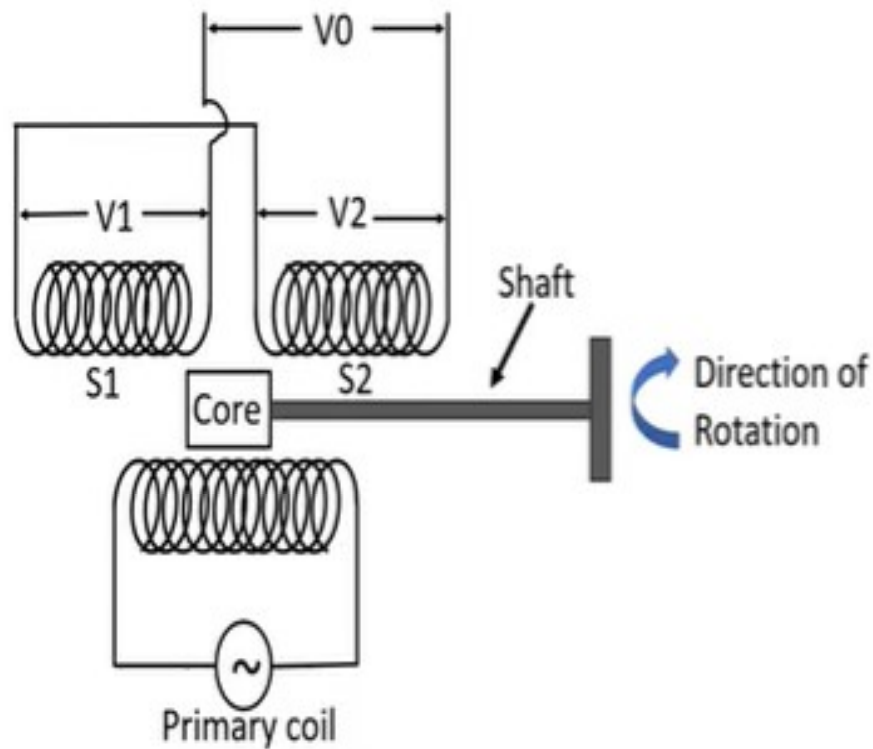The displacement versus output voltage of an RVDT



- Advantages
- High stability
- Long life
- Compact
- Strong
- Low cost
- Resolution infinity
- High Linearity

- **Disadvantages**

- Screw type core- Chance for friction and leads to wear and tear
- Only detected the angles in between -40 and +40. Other ranges will not be detected.

Thank you