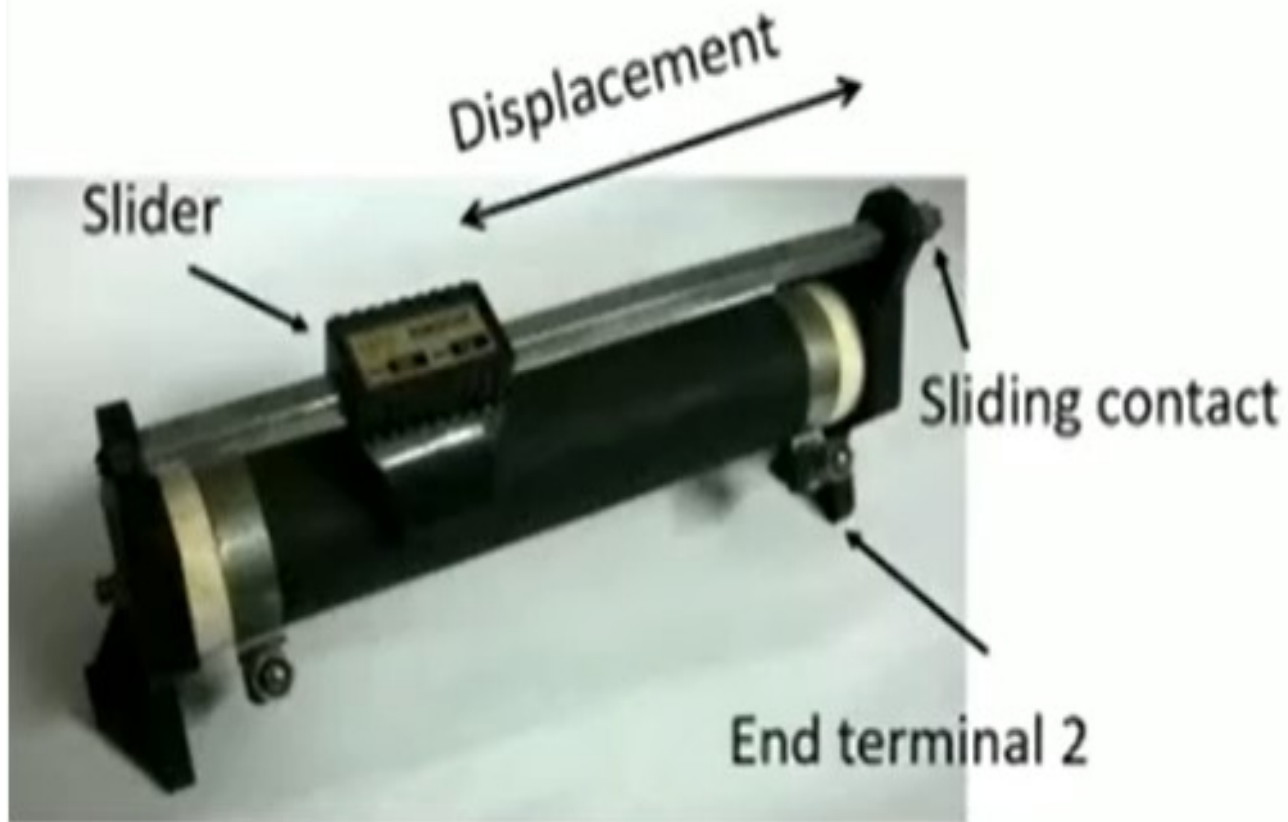


Potentiometer and Loading Effect


Riya Jacob K

Assistant Professor on Contract
Dept of Computer Applications


- A potentiometer is a device in which a resistive wire or material is wound on an insulating core.



End terminal 1

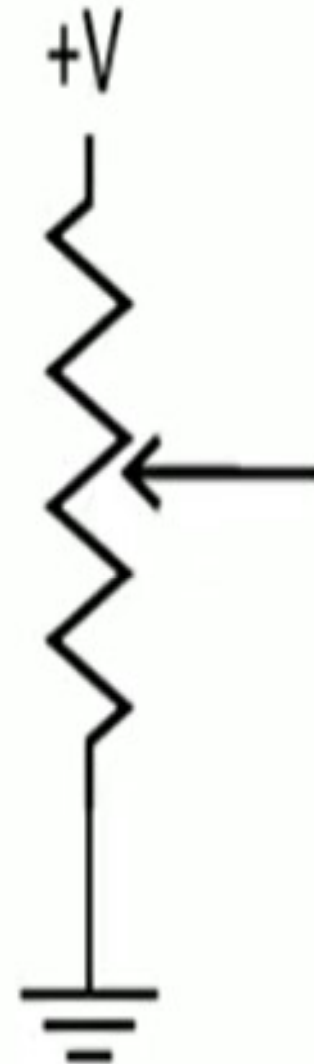


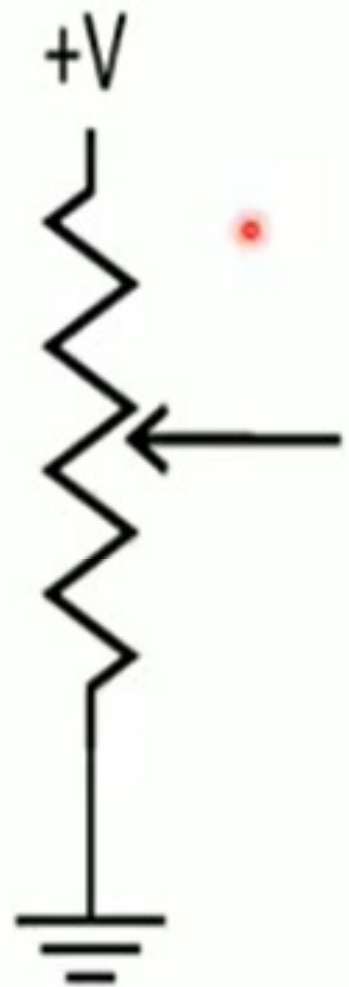- The movement of sliding contact may be translational (straight), rotational or combination of these two.
- A dc or ac voltage source is used to energise the potentiometer.



- The voltage across the slider contact and ground

$$V_o = \frac{X_o \cdot V}{X_t}$$

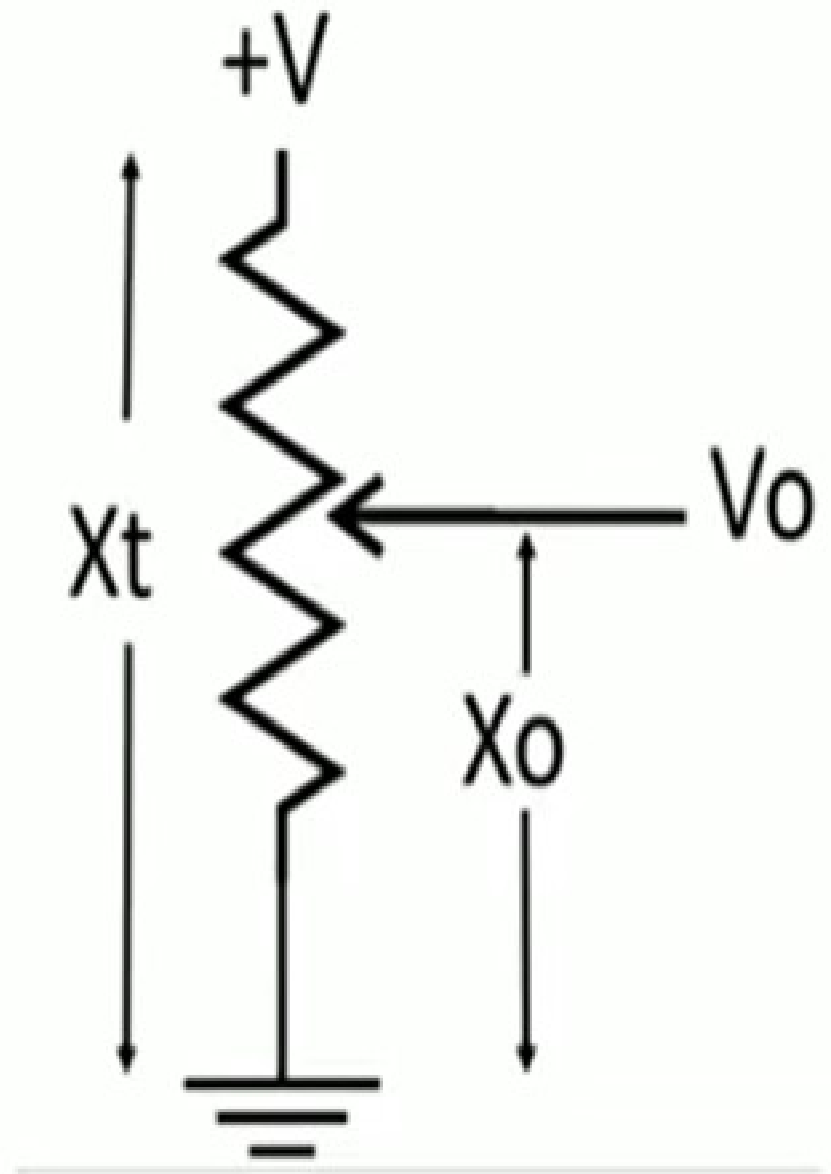


- If the total resistance of the potentiometer is R_t and R_o is the resistance of the portion of the potentiometer from the slider to electrical ground.

- Then the voltage


$$V_o = \frac{R_o \cdot V}{R_t}$$

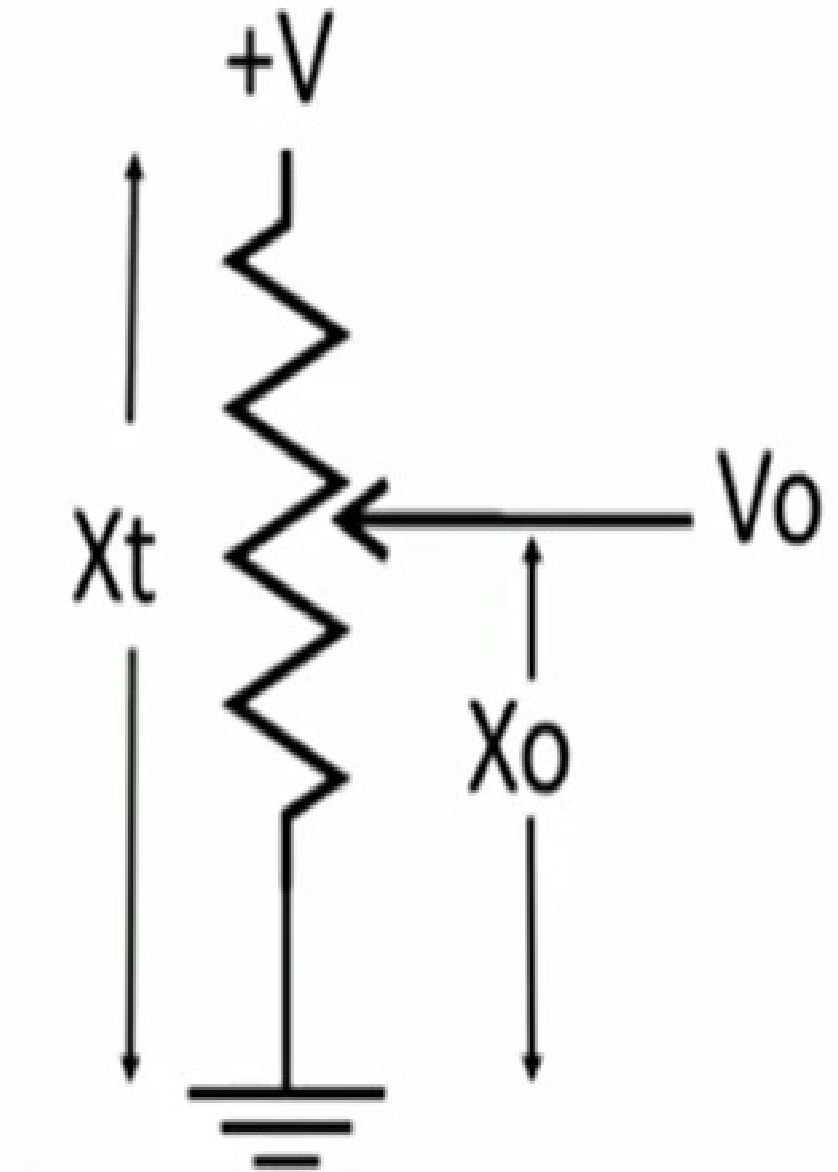- The voltage V_o is proportional to the displacement.





Loading effect on Potentiometer

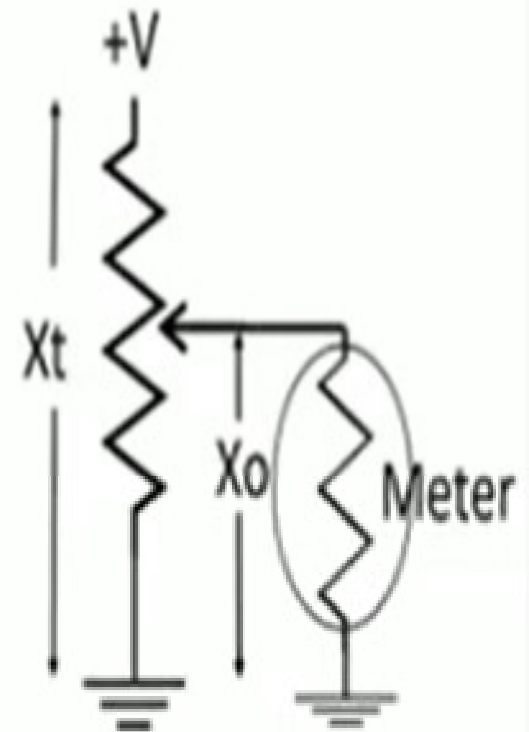- The output of the potentiometer is generally connected to the input of an amplifier or measuring device.
- The input resistance of the amplifier or measuring device also affects the voltage between the slider contact and ground.
- This effect is known as loading effect of the potentiometer.




- R_m is meter resistance
- The effective resistance R_e is $R_e = R_o || R_m$
- $R_e = \frac{R_o R_m}{(R_o + R_m)}$
- $V_e = \frac{R_e V}{(R_t - R_o) + R_e}$
- (Since the resistance between the sliding contact and +V is $(R_t - R_o)$ and that of slider contact and ground terminal in this case is R_e).

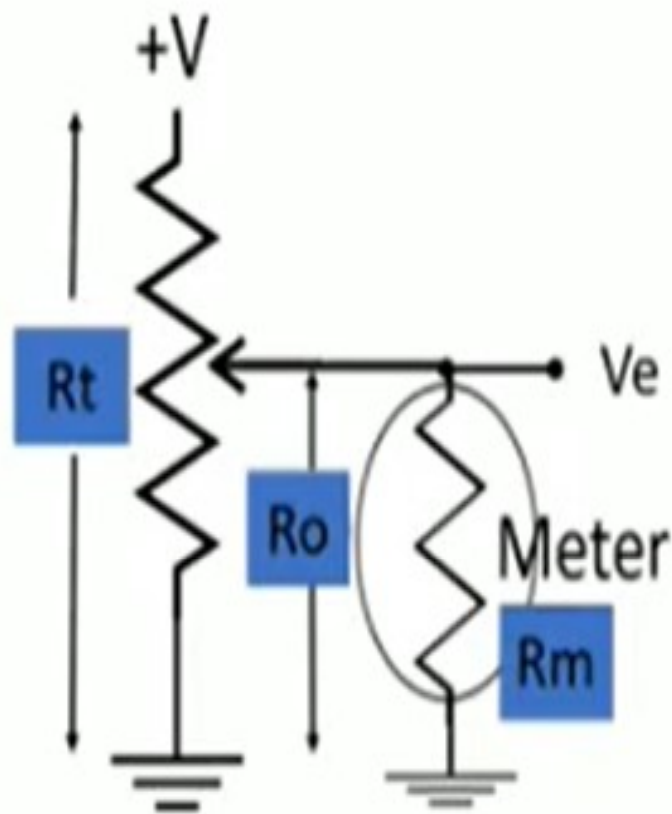

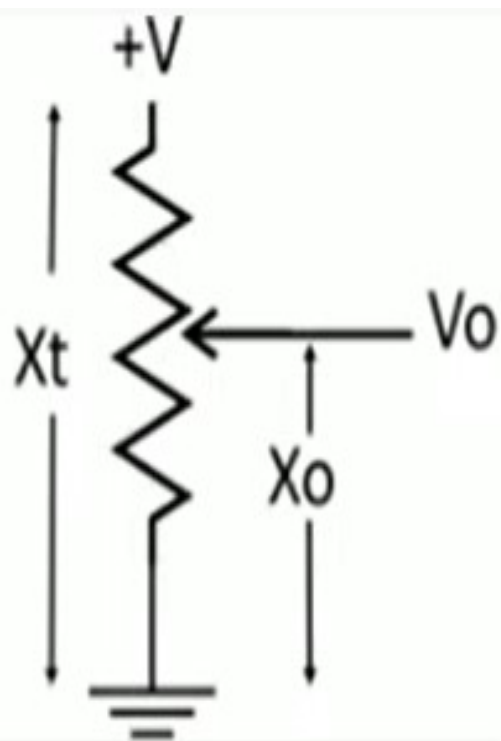

$$V_o = \frac{R_o \cdot V}{R_t}$$

$$E = \frac{V_e - V_o}{V_o}$$

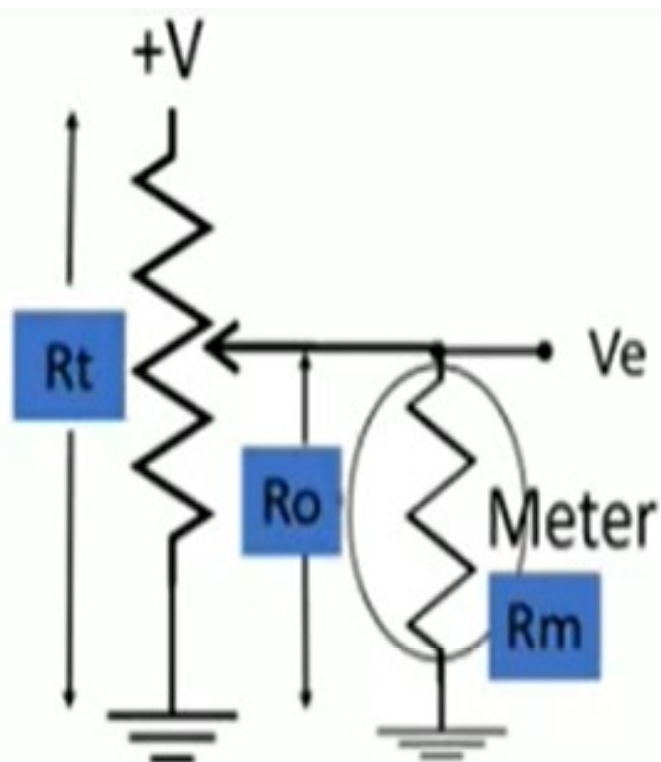

$$V_e = \frac{R_e V}{(R_t - R_o) + R_e}$$

- Error = $\frac{\text{Measured Value} - \text{True Value}}{\text{True Value}}$

i.e.,

$$E = \frac{V_e - V_0}{V_0}$$

Thank you