

Comparison of the three transistor configurations

&

Advantages of the CE configuration

Prepared By
Anne Jose M
Department of Physics,
Little Flower College, Guruvayoor

Comparison of the three transistor configurations

Parameter	CB	CE	CC
Input resistance			
Output resistance			
Current gain			
Voltage gain			
Power gain			

Input Resistance

	CB	CE	CC
Input is applied between	Emitter and base	Base and emitter	Base and collector
	Forward biased	Forward biased	Reverse biased
Input resistance	Low	Low	Very high
	$r_{in} = \frac{\Delta V_{EB}}{\Delta I_E}$	$r_{in} = \frac{\Delta V_{BE}}{\Delta I_B}$	$r_{in} = \frac{\Delta V_{BC}}{\Delta I_B}$
	About 100Ω	About 750Ω	About 750kΩ


Comparison of the three transistor configurations

Parameter	CB	CE	CC
Input resistance	Low (about 100Ω)	Low (about 750Ω)	Very large (about $750\text{ k}\Omega$)
Output resistance			
Current gain			
Voltage gain			
Power gain			

Output Resistance

	CB	CE	CC
Output is applied between	Collector and base	Collector and emitter	Emitter and collector
	Reverse biased		
Output resistance	Very large	Large	Low
	$r_{out} = \frac{\Delta V_{CB}}{\Delta I_C}$	$r_{out} = \frac{\Delta V_{CE}}{\Delta I_C}$	$r_{out} = \frac{\Delta V_{EC}}{\Delta I_E}$
	About 450kΩ	About 45 kΩ	About 50Ω

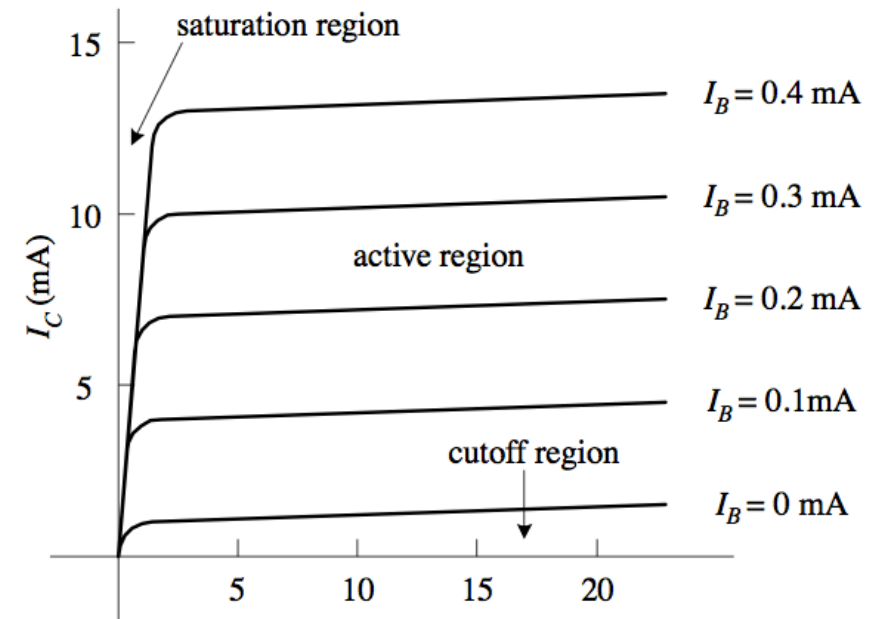Output characteristics of CE configuration



Comparison of the three transistor configurations

Parameter	CB	CE	CC
Input resistance	Low (about 100Ω)	Low (about 750Ω)	Very large (about $750\text{ k}\Omega$)
Output resistance	Very large (about $450\text{ k}\Omega$)	Large (about $45\text{ k}\Omega$)	Small (50Ω)
Current gain			
Voltage gain			
Power gain			

CURRENT GAIN

	CB	CE	CC
Current gain	$\alpha = \frac{\Delta I_C}{\Delta I_E}$	$\beta = \frac{\Delta I_C}{\Delta I_B}$	$\gamma = \frac{\Delta I_E}{\Delta I_B}$
	Almost unity (less than 1)	Large (ranges from 20 to 500)	Large (\approx current gain of CE configuration)
Voltage gain	Large (About 150)	Large (About 500)	Almost unity (less than 1)
Reason	Very high output circuit resistance		Very low output resistance
Power Gain	Large	Very large	Small

Comparison of the three transistor configurations

Parameter	CB	CE	CC
Input resistance	Low (about 100Ω)	Low (about 750Ω)	Very large (about $750\text{ k}\Omega$)
Output resistance	Very large (about $450\text{ k}\Omega$)	Large (about $45\text{ k}\Omega$)	Small (50Ω)
Current gain	Almost unity (less than 1)	Large (ranges from 20 to 500)	Large (ranges from 20 to 500)
Voltage gain	Large (about 150)	Large (about 500)	Almost unity (less than 1)
Power gain	Large	Very large	Small

Advantages of the CE configuration

CE transistor configuration is used in about 90 to 95% of all transistor applications.

- It has high current gain which may range from 20 to 500.
- It has the highest voltage gain and power gain of three transistor connections.
- It has moderate output to input impedance ratio (about 50). This makes CE configuration an ideal one for coupling between various transistor stages.

THANK YOU